



PDHonline Course E277 (4 PDH)

Operational Amplifier Stability and Common-Mode Noise Rejection

Instructor: George Rutkowski, PE

2020

PDH Online | PDH Center

5272 Meadow Estates Drive
Fairfax, VA 22030-6658
Phone: 703-988-0088
www.PDHonline.com

Appendix C

The Noninverting Amplifier


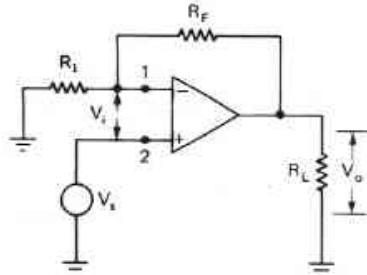


Figure 1C Op Amp wired to work as a Noninverting Amplifier


The closed-loop voltage gain of the noninverting Op Amp configuration can be selected with the following equation:

$$A_v \approx \frac{R_F}{R_1} + 1$$

This equation's derivation can be worked through with Ohm's and Kirchoff's laws while including the Op Amp's very large open-loop gain A_{VOL} . Because V_{id} is so small compared to signal voltage V_s , this V_s is effectively across resistor R_1 . It follows then that the signal current I is the same through resistors R_1 and R_F because the resistance looking into inputs 1 and 2 is relatively very large

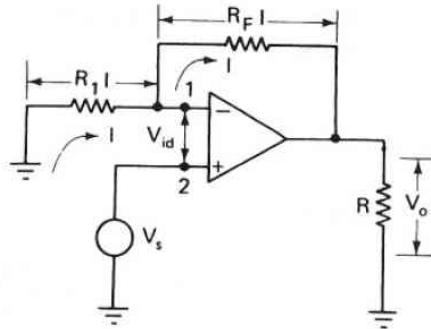

(a)

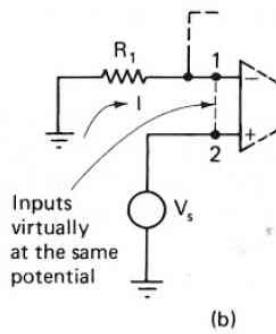

(b)

Figure 1C Current Paths resulting from the Applied Input Signal V_s

In other words, resistors R_1 and R_F are effectively in series and that the sum of the voltages across them is the output voltage V_o . Therefore we can show that the voltage gain is:

$$A_v = \frac{V_o}{V_s} \cong \frac{(R_F + R_1)I}{R_1 I} = \frac{R_F + R_1}{R_1} = \frac{R_F}{R_1} + 1.$$

The current direction shown in this figure is instantaneous when the input signal voltage V_s is positive with respect to ground at the same instant.