



PDHonline Course E431 (2 PDH)

The Square Root of Three ($\sqrt{3}$) in Electrical Calculations

Instructor: David A. Snyder, PE

2020

PDH Online | PDH Center

5272 Meadow Estates Drive
Fairfax, VA 22030-6658
Phone: 703-988-0088
www.PDHonline.com

An Approved Continuing Education Provider

The Square Root of Three ($\sqrt{3}$) in Electrical Calculations

David A. Snyder, PE

Table of Contents

Introduction.....	3
$\sqrt{3}$ Relationship of Three-Phase Voltages.....	4
Figure 1 – 480Y/277V Wye-Delta Voltage Relationship.....	4
Figure 2 –Wye-Delta Voltage Relationship – Right Triangle Geometry	5
Figure 3 – 208Y/120V Wye-Delta Voltage Relationship.....	6
$\sqrt{3}$ In Three-Phase Line Current Calculations	6
Table 1 – Types of Loads for Line Current Examples.....	7
Delta-Connected, Three-Phase, Resistance Loads	7
Balanced, Delta-Connected, Three-Phase, Resistance Loads.....	7
Figure 4 – 30 KW, Balanced, Delta-Connected, Three-Phase, Resistance Load	7
Figure 5 – Voltage V_{ab} and Current I_{ab} in Delta-Connected, Resistance Load	8
Figure 6 – Relationships between Three-Phase Voltages and Currents for Resistance Load	8
Figure 7 – 30 KW, Balanced, Delta-Connected, Three-Phase, Resistance Load at 480 V	9
Unbalanced, Delta-Connected, Three-Phase, Resistance Loads.....	10
Figure 8 – 30 KW, Unbalanced, Delta-Connected, Three-Phase, Resistance Load	10
Figure 9 – 30 KW, Unbalanced Three-Phase Resistance Load at 480 V	11
Balanced Three-Phase Load as Three Single-Phase Loads	12
Unbalanced Three-Phase Load as Three Single-Phase Loads.....	13
Wye-Connected, Three-Phase, Resistance Loads.....	13
Balanced, Wye-Connected, Three-Phase, Resistance Loads without Neutral Connection ..	13
Figure 10 – 10 KW, Balanced, Wye-Connected, Three-Phase, Resistance Load, without Neutral Connection	14
Balanced, Wye-Connected, Three-Phase, Resistance Loads with Neutral Connection	15
Figure 11 – 10 KW, Balanced, Wye-Connected, Three-Phase, Resistance Load, with Neutral Connection	15
Figure 12 – 10 KW, Balanced, Wye-Connected, Three-Phase Load at 480 V.....	16
Unbalanced, Wye-Connected, Three-Phase, Resistance Loads with Neutral Connection ...	16
Figure 13 – 10 KW, Unbalanced, Wye-Connected, Three-Phase, Resistance Load, with Neutral Connection	17
Figure 14 – 10 KW, Unbalanced, Wye-Connected, Three-Phase, Resistance Load at 480 V	18
$\sqrt{3}$ In Three-Phase Transformer Banks	18
Closed-Delta Transformer Banks	18
Figure 15 – Three-Phase Delta-Connected Transformer Banks at 240 V	19
Figure 16 – Currents in Three-Phase Delta-Connected Transformer Banks at 240 V	20
Open-Delta Transformer Banks.....	21
$\sqrt{3}$ In Three-Phase Voltage-Drop Calculations.....	22
Figure 17 – The Square Root of Three in Balanced Three-Phase Voltage-Drop Calculations	23
In Closing.....	24
Abbreviations.....	24

Additional Reading 24

Introduction

Everyone knows that we divide the KW or KVA of a balanced three-phase load by the square root of three ($\sqrt{3}$) in order to get the full-load amps required by that load, but many people don't realize why we do that. The square root of three is also used in voltage drop calculations for balanced three-phase loads. The square root of three is the relationship between the two voltages in a 480Y/277V system (Figure 1 on page 4) and between the two voltages in a 208Y/120V system (Figure 3 on page 6). It is the 120° separation between each of the three-phase voltages that is the driving force behind our use of the square root of three in electrical calculations for three-phase systems.

This course presents solutions to three-phase line current problems by using easily-visualized vector addition and subtraction, with some simple mathematics and formulas. For those Readers who prefer more-mathematical solutions, or who want an alternative method for balanced and unbalanced three-phase circuits, the Author suggests PDH Online Course *E336 Calculating Currents in Balanced and Unbalanced Three Phase Circuits*, listed in the Additional Reading section beginning on page 24.

The use of the square root of three will be discussed in the following applications: relationship of three-phase voltages, three-phase line current calculations, three-phase transformer bank ratings, and three-phase voltage-drop calculations. In this course, phase rotation is assumed to be A-B-C, in the counter-clockwise direction in vector space. Unless otherwise indicated, it is assumed that the line conductors from the power source to the loads have no resistance or reactance. Power factor will be ignored wholesale in this course, such as when calculating available current based on a transformer's KVA rating.

This course has several scaled drawings or figures. When printing a scaled PDF, choose "Actual Size" or a "Custom Scale" of 100% for accurate results. The Reader is encouraged to use a decimal scale or ruler (the decimal edge of a framing square will do, in a pinch) to measure the results illustrated in the scaled figures

$\sqrt{3}$ Relationship of Three-Phase Voltages

The square root of three is the ratio of the line-to-line (phase-to-phase) voltage (480 V) to the line-to-neutral (phase-to-neutral) voltage (277 V) in three-phase power systems. Figure 1 below illustrates this relationship.

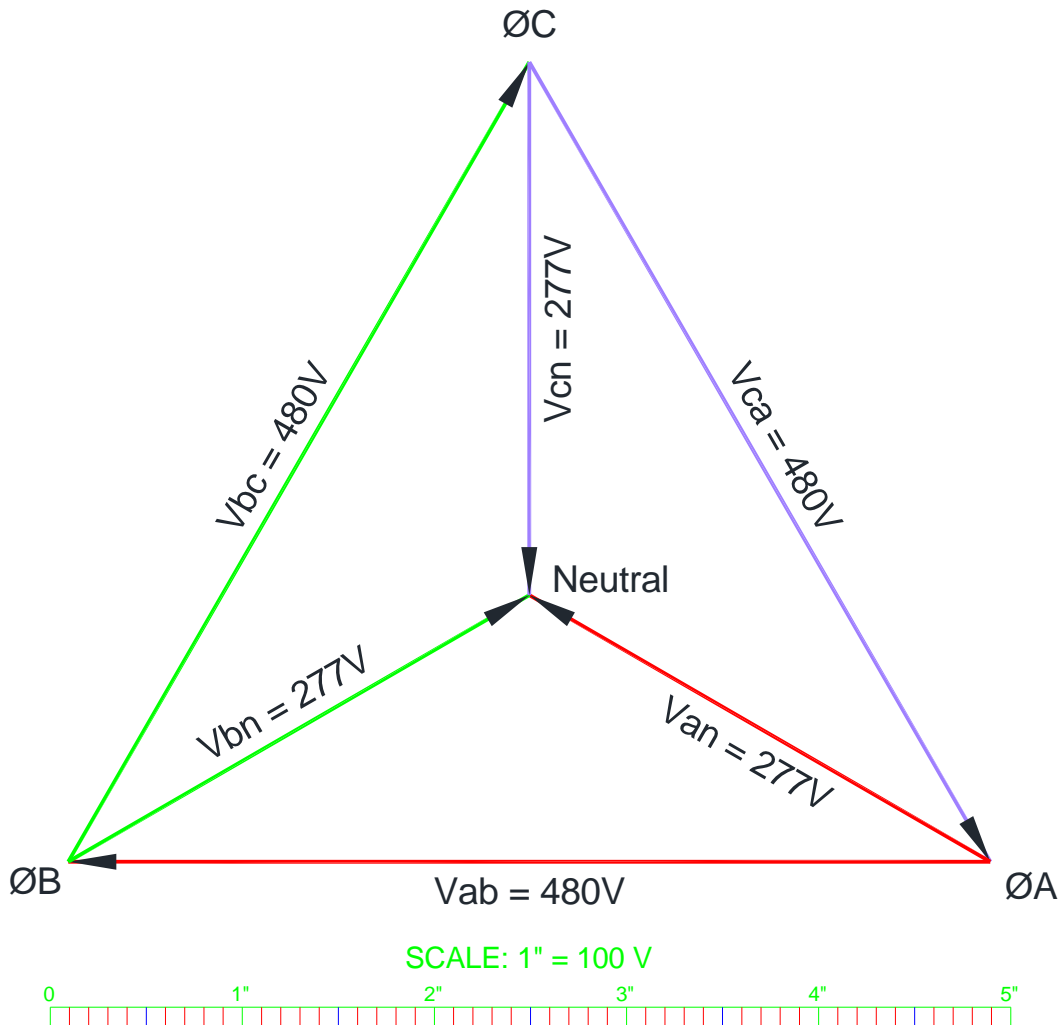


Figure 1 - 480Y/277V Wye-Delta Voltage Relationship

The voltage relationship between 277 V wye and 480 V delta from Figure 1 can be thought of as simple right-triangle geometry, where the hypotenuse is 277 V and the adjacent side to the 30° angle is half of 480 V, or 240 V. The length of the short side opposite the 30° angle is of no concern for this exercise. Figure 2 below is the bottom portion of Figure 1 above.

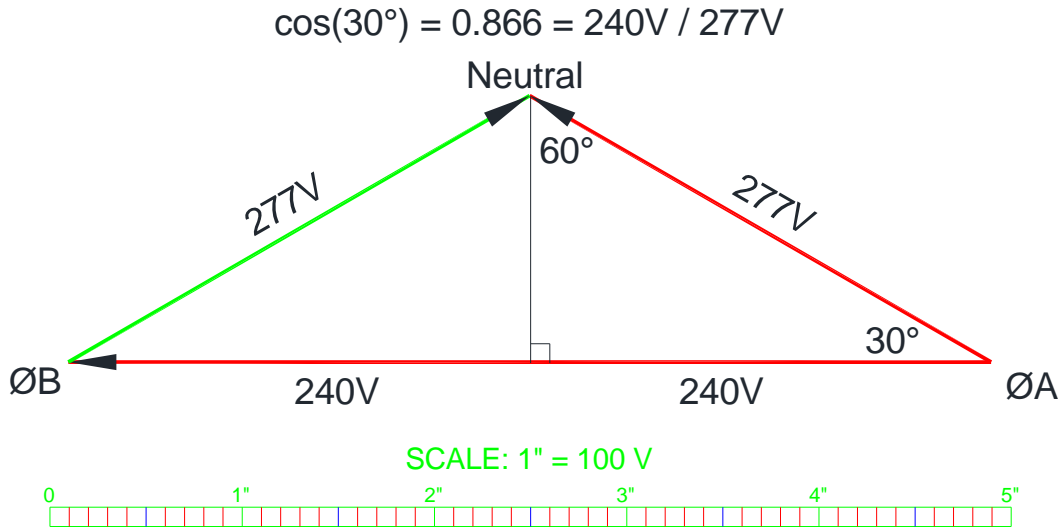


Figure 2 -Wye-Delta Voltage Relationship - Right Triangle Geometry

As shown in Figure 2, the length of the 240 V side of both right triangles is related to the length of the 277 V sides by the cosine of 30° , which is 0.866. Alternatively, we could have used the 60° corner for reference in Figure 2 and stated that the relationship between 240 V and 277 V was defined by: $\sin(60^\circ) = 0.866 = 240 \text{ V} / 277 \text{ V}$ to get the same result. The value of 0.866 is actually $\sqrt{3} / 2$, as one might expect from the voltages shown in Figure 2.

The square root of three also comes into play for the voltage applied to a wye-delta motor. See PDH Online Course *E413 Wye-Delta Motor Starters*, listed in the Additional Reading section beginning on page 24.

The same square root of three ($\sqrt{3}$) relationship between the line-to-line voltage and line-to-neutral voltage holds true for 280Y/120V as shown in Figure 3 below

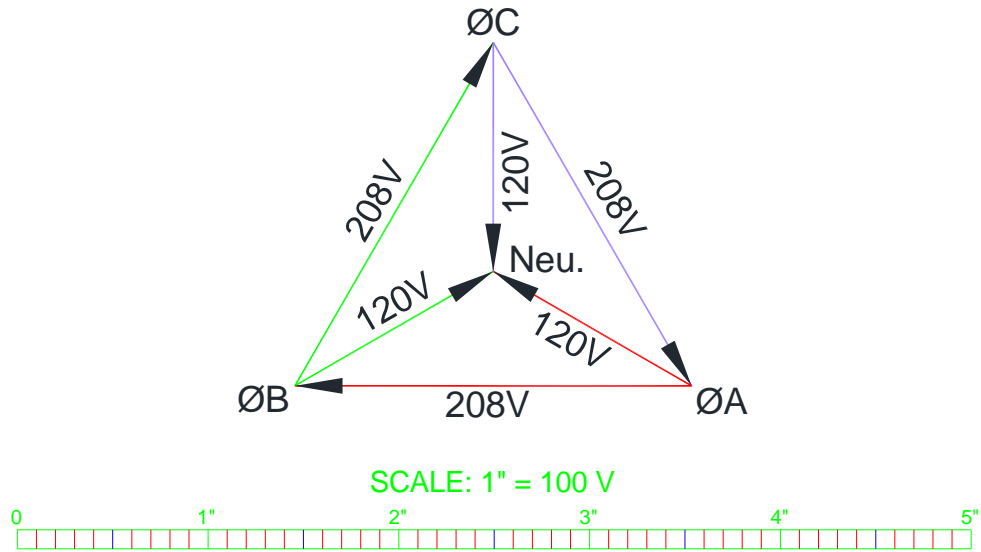


Figure 3 – 208Y/120V Wye-Delta Voltage Relationship

The square root of three ($\sqrt{3}$) relationship holds true for all three-phase power systems, including 400Y/230V and 600Y/347V. See PDH Online Course *E427 Standard AC System Voltages (600 V and Less)*, listed in the Additional Reading section beginning on page 24, for more information on various AC system voltages.

Having discussed the use of the square root of three in the relationship of three-phase voltages, let's move on to our next topic, the use of the square root of three in three-phase line current calculations.

$\sqrt{3}$ In Three-Phase Line Current Calculations

The line current is the current in the power conductors going to the load. The line current, therefore, is the current used in sizing the conductors for a circuit, as well as for sizing the protective device, such as a breaker or fuse. In this section, and associated sub-sections, we will see that the square root of three can be used to determine the line current for balanced, three-phase loads, but not unbalanced, three-phase loads. As previous stated, it is assumed that the line conductors from the power source to the loads have no resistance and no reactance.

In this section, we will look at delta-connected and wye-connected resistance three-phase loads. The following table can serve as a quick guide in finding the appropriate section:

Type of Load for Three-Phase Line Current Examples	Page #
Balanced, Delta-Connected, Three-Phase, Resistance Loads	7
Unbalanced, Delta-Connected, Three-Phase, Resistance Loads	10
Balanced, Wye-Connected, Three-Phase, Resistance Loads without Neutral Connection	13
Unbalanced, Wye-Connected, Three-Phase, Resistance Loads with Neutral Connection	16

Table 1 - Types of Loads for Line Current Examples

Impedance loads are not discussed in this course, but the concepts are basically the same as for resistance loads. The main difference for impedance loads is that the current vectors will lag behind the voltage vectors by the power factor angle, for lagging power factors, of course.

Delta-Connected, Three-Phase, Resistance Loads

Let's start by looking at balanced, delta-connected, three-phase, resistive loads, then we will move on to unbalanced, delta-connected, three-phase, resistive loads in a later section.

Balanced, Delta-Connected, Three-Phase, Resistance Loads

Figure 4 shows a balanced, three-phase resistance load connected in delta and powered by a 480 V, 3-phase, 3-wire delta source. This is known as a balanced, three-phase load because all three of the loads are equal to each other: 10 KW, in this example. Since there are three 10 KW loads, the total load is 30 KW in Figure 4. When calculating the current flow to a balanced 30 KW load at 480 V, three-phase, we simply divide the total load by the applied line-to-line voltage and the square root of three, thusly: $30,000 \text{ W} / (480\text{V} * \sqrt{3}) = 36.1 \text{ A}$. This is the value of each of the line currents I_a , I_b , and I_c , but they are 120° apart from each other.

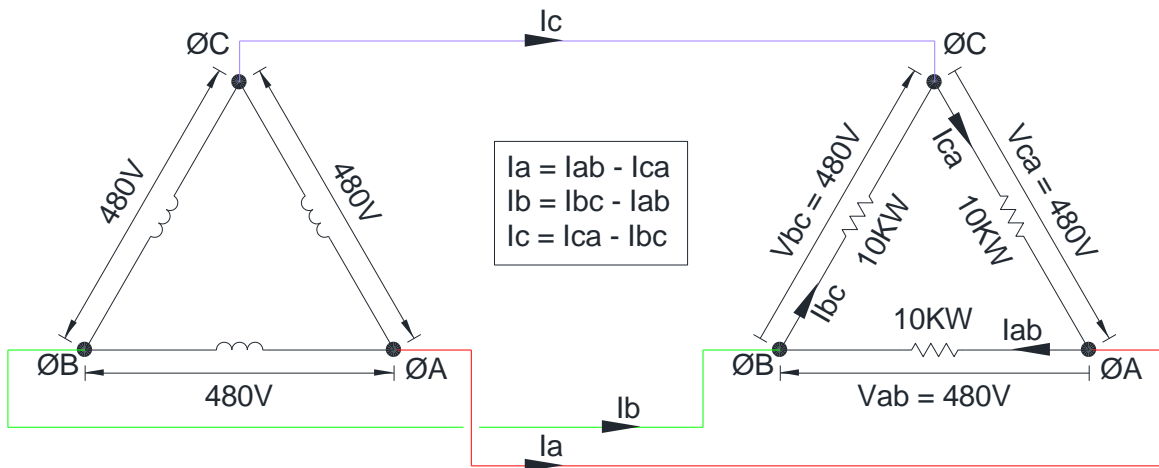


Figure 4 - 30 KW, Balanced, Delta-Connected, Three-Phase, Resistance Load

Where does the $\sqrt{3}$ value come from – why do we include it in this calculation? It is a direct result of the geometry of an equilateral triangle, in which all three sides are equal, and the fact that the line current (I_a) going to each connection of the load is equal to the vector sum of the currents (such as $I_{ab} + -I_{ca}$) at that connection. To visualize this, look at Figure 4, in which the current I_a coming from phase A of the power source is equal to the sum of the $+I_{ab}$ and $-I_{ca}$. This does not imply a simple addition of the magnitudes of the currents in each leg to get the total, but, instead, it is the vector sum of $+I_{ab}$ and $-I_{ca}$, as illustrated in Figure 7 on page 9. Let's choose one of the three legs at random, the one between phase A and Phase B. The current in that leg and in each leg of the balanced load is $10,000 \text{ W} / 480\text{V} = 20.83 \text{ A}$. The angle or direction of that current is in the same angle or direction as the applied voltage, since the load is composed of resistance only, for this example. Figure 5 below shows the angle of V_{ab} and I_{ab} for the 10 KW load connected between phase A and phase B of the power source.

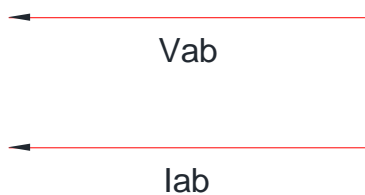


Figure 5 – Voltage V_{ab} and Current I_{ab} in Delta-Connected, Resistance Load

Since voltage V_{ab} in Figure 5 is applied to a resistance, not an inductance, the current vector is in the same direction as the applied voltage. As mentioned previously, if the load were composed of impedances instead of pure resistances, the current and voltage vectors in each phase would be separated from each other by the impedances' power factor angle.

Notice that we didn't use the square root of three to calculate the current in one phase-to-phase load inside the delta-connected load. The current value of 20.83 A is the same for each of three legs, but the direction of each current is different in each case, since the vector direction of the applied voltage is different in each case. See Figure 6 below for vector representations of the three applied voltages and three resulting currents for the balanced 30 KW load we are presently discussing.

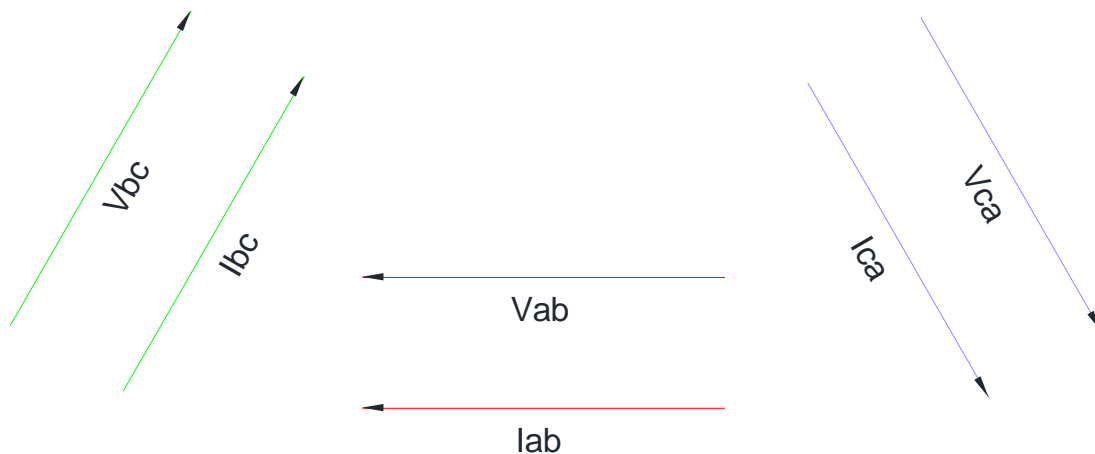


Figure 6 – Relationships between Three-Phase Voltages and Currents for Resistance Load

The magnitudes of the currents and voltages are not shown in Figure 5 and Figure 6, just the directions of the vectors.

As we can see in Figure 4 on page 7, the line current I_a going from phase A of the three-phase power source is equal to the delta current vector I_{ab} minus delta current vector I_{ca} . The resulting vector is illustrated at the bottom left-hand of Figure 7 below. The results for line current vectors I_b and I_c are also shown in that figure. Since this a balanced load, the line current values are the same in each line conductor (36.1 A), but they are in different directions, also separated from each other by 120° .

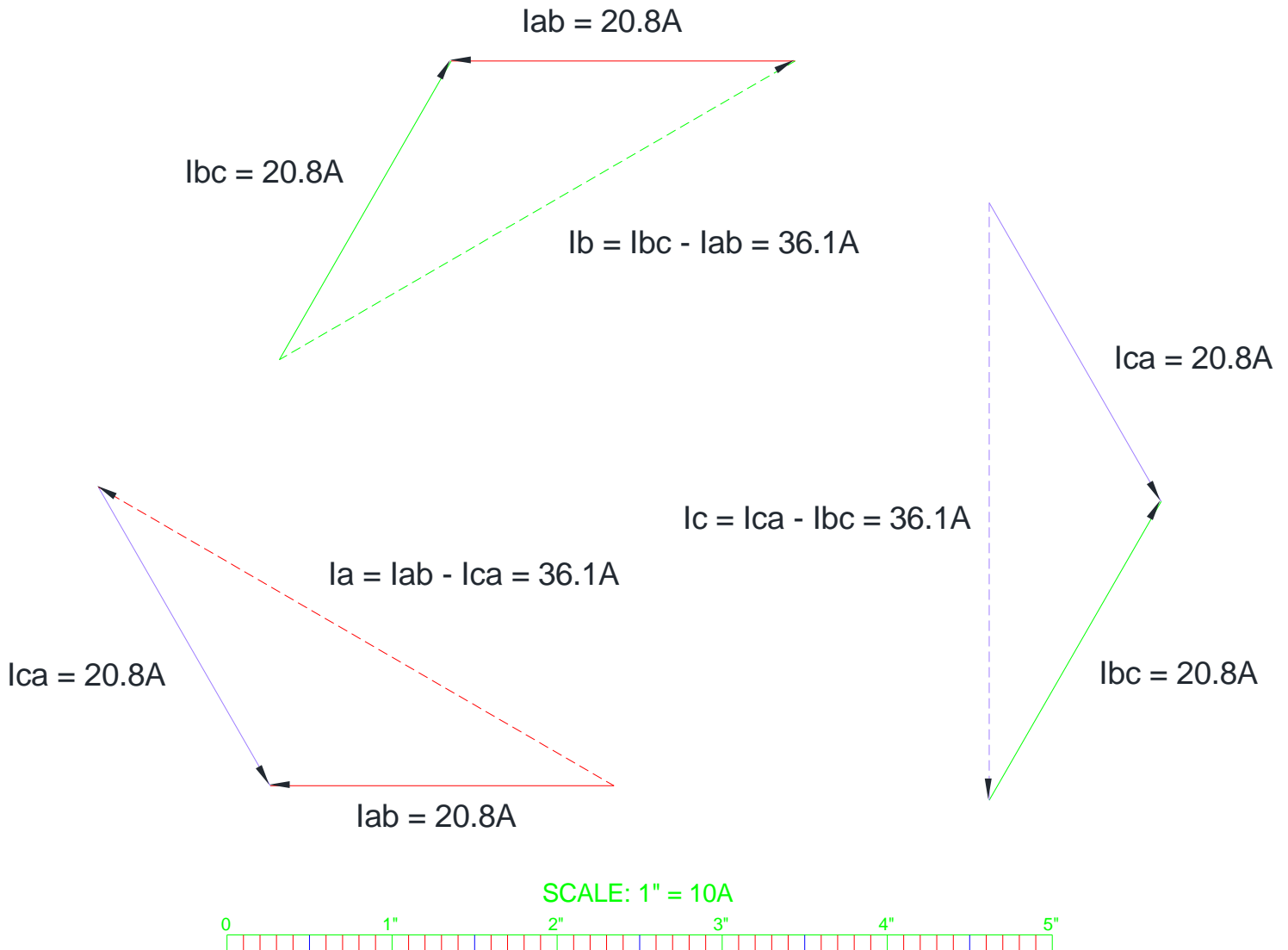


Figure 7 - 30 KW, Balanced, Delta-Connected, Three-Phase, Resistance Load at 480 V

For balanced, three-phase loads, we don't have to do any if this vector manipulation to determine the resulting line currents, we can just divide the total load by the line-to-line voltage (480 V) and the square root of three. This is not true for unbalanced three-phase loads.

Unbalanced, Delta-Connected, Three-Phase, Resistance Loads

Unbalanced three-phase loads are largely ignored in technical publications and design guides, but such installations are not uncommon, such as eight 1,000 W lighting fixtures on a high-mast lighting pole powered by 480 V, three-phase. It is not accurate to divide 8,000 W by 480 V and $\sqrt{3}$ to come up with a line current of 9.6 A, but it is a close-enough approximation to select the proper breaker and conductor size for this circuit. Let's consider a similar example with a purely resistive, unbalanced, delta-connected three-phase load.

Figure 8 shows an unbalanced, three-phase 30 KW load connected in delta and powered by a 480 V, 3-phase, 3-wire delta source. Even though the total load is 30 KW, the same as in the previous example, the load is not balanced between the three phases. The individual loads in the three legs in this example are 5 KW, 5 KW, and 20 KW.

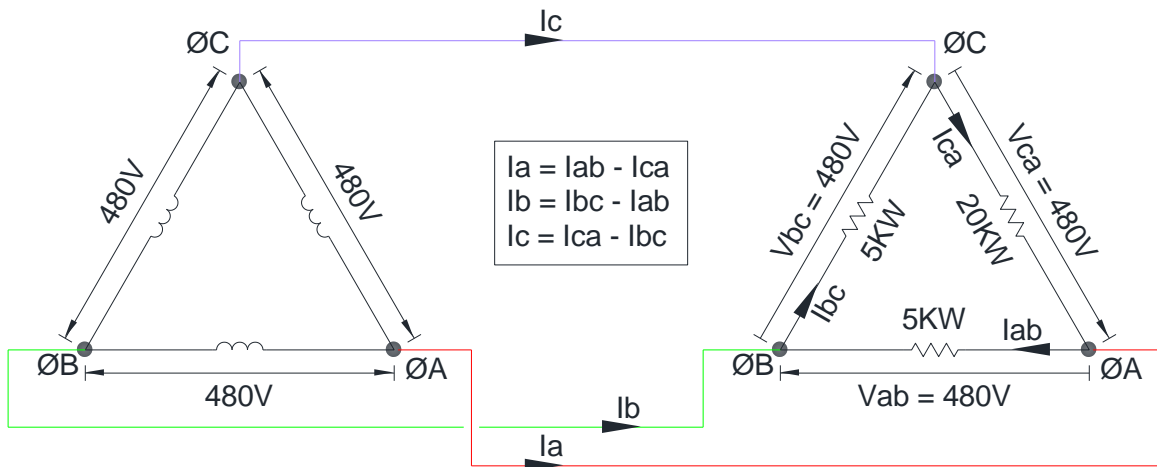


Figure 8 - 30 KW, Unbalanced, Delta-Connected, Three-Phase, Resistance Load

Looking at the load connected between phase A and phase B, the current in this leg is $5 \text{ KW} / 480 \text{ V} = 10.4 \text{ A}$. This is also true of the 5 KW load connected between phase B and phase C. The 20 KW load connected between phase C and phase A will have a current of $20 \text{ KW} / 480 \text{ V} = 41.7 \text{ A}$. Figure 9 below shows us how these three current vectors add up to give us line currents of $I_a = 47.8 \text{ A}$, $I_b = 18.0 \text{ A}$, and $I_c = 47.8 \text{ A}$, a significant departure from the line current values of 36.1 A shown in Figure 7 on page 9.

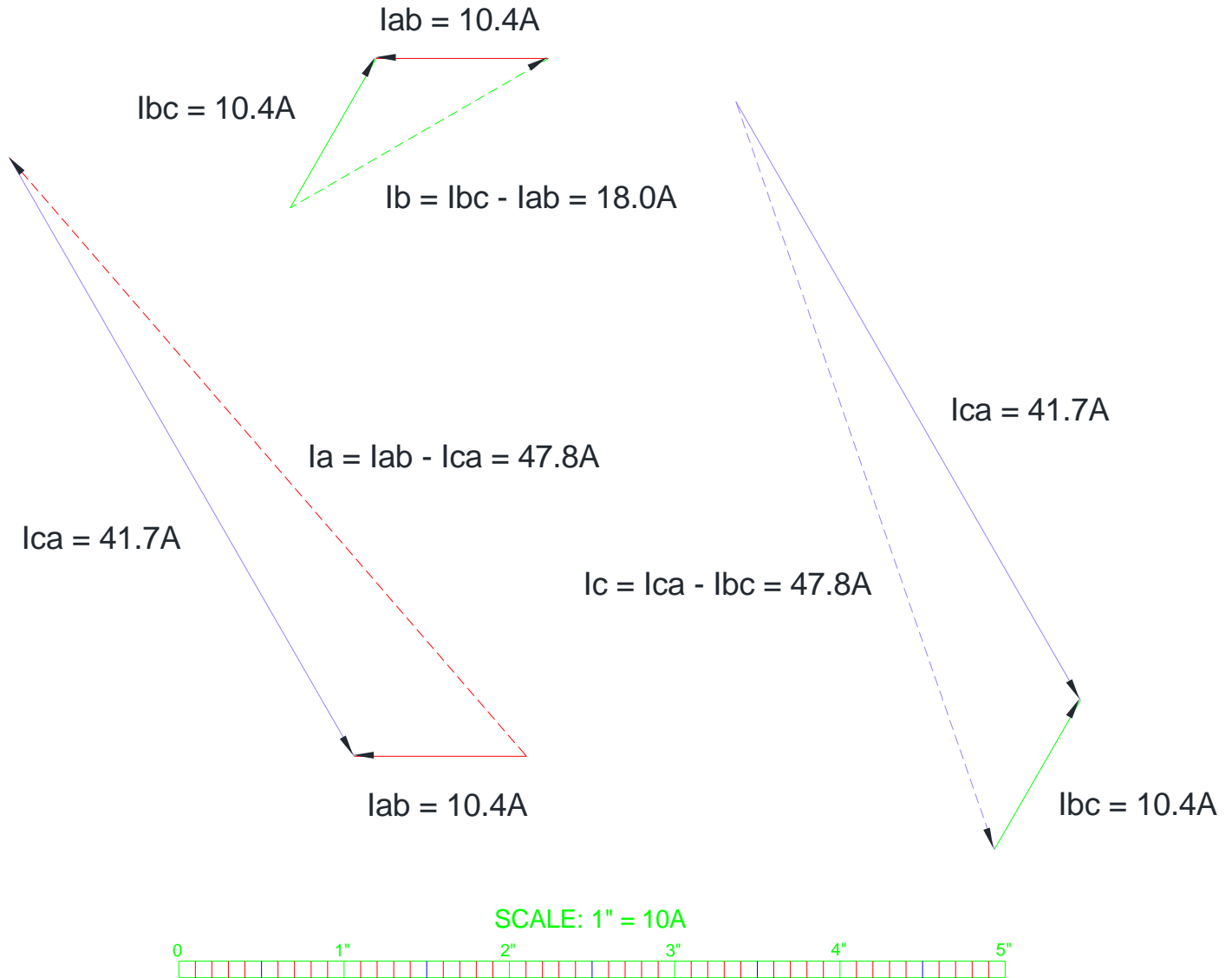


Figure 9 - 30 KW, Unbalanced Three-Phase Resistance Load at 480 V

As can be seen in Figure 9, the line currents can be significantly different for an unbalanced 30 KW load, when compared to a balanced 30 KW load. Simply dividing 30 KW by 480 V and $\sqrt{3}$ does not give an accurate representation of the line current for an unbalanced, three-phase load.

All three-phase loads, whether balanced or unbalanced, are three single-phase loads. It is not really accurate to think of our resistance heater as being a 30 KW heater, since the actual KW rating varies as the square of the input voltage – it is more accurate to think of it as being three resistors. Before we proceed to wye-connected three-phase loads, let's consider the fact that all three-phase loads are actually three single-phase loads.

Balanced Three-Phase Load as Three Single-Phase Loads

If a typical, balanced resistance heater is rated 30 KW at 480 V, three-phase, then it would be rated at a much lower KW value at 208 V, three-phase; a value that would be proportional to the squares of the two voltages in question:

$$\text{Ratio} = (208)^2 : (480)^2 = 43,264 : 230,400 = 0.188 : 1$$

Applying this ratio to the 30 KW heater at 480 V, three-phase gives us a new KW value at 208 V, three-phase:

$$\text{New KW} = 30 \text{ KW} * 0.188 = 5.63 \text{ KW}$$

This concept might be easier to see if we convert the so-called 30 KW heater into its three resistance values. Each of the three legs of the heater is rated 10 KW when 480 V is applied across the leg in question, as shown in Figure 4 on page 7. Ohm's law tells us that:

$$P = V * I = V * (V / R) = V^2 / R$$

We know the power P is 10 KW for one leg and the voltage V is 480 V across the leg, so:

$$10,000 = (480)^2 / R$$

Rearranging the above equation:

$$R = (480)^2 / 10,000 = 23 \Omega$$

What would be the current through 23 Ω with 480 V applied? It would be $480 / 23 = 20.8 \text{ A}$, which is the same value for each of the leg currents in Figure 7 on page 9.

What would be the current through 23 Ω with the lower voltage of 208 V applied? It would be $208 / 23 = 9 \text{ A}$, which is simply a linear relationship to 20.8 A at 480 V, but when multiplying the currents by the associated voltages, there is a significant difference in the KW ratings of the heater at the two different voltages. We already know that each leg is a 10 KW load at 480 V, but the same resistance will have a much lower KW value at 208 V:

$$P = V * I = 208 \text{ V} * 9 \text{ A} = 1,872 \text{ W}$$

The total for three resistances:

$P = 3 * 1,872 \text{ W} = 5,616 \text{ W}$, which we have already calculated near the beginning of this section to be 5.63 KW. If a calculator is used instead of relying on the rounded-off values in this example, the results will match up more precisely.

Unbalanced Three-Phase Load as Three Single-Phase Loads

Looking back at the unbalanced 30 KW load in Figure 8 on page 10, composed of one 20 KW leg and two 5 KW legs, the one 20 KW load at 480 V is actually a resistance of:

$$R = (480)^2 / 20,000 = 11.5 \Omega \text{ (half the 10 KW resistance)}$$

The current in the 20 KW leg is $480 \text{ V} / 11.5 \Omega = 41.7 \text{ A}$ (twice the 10 KW current), as previously shown in Figure 9 on page 11.

Each of the two 5 KW legs has a resistance value of:

$$R = (480)^2 / 5,000 = 46 \Omega \text{ (twice the 10 KW resistance)}$$

The current in each of the 5 KW legs is $480 / 46 = 10.4 \text{ A}$, as previously shown in Figure 9 on page 11.

Let's get back to our discussion of three-phase resistance loads. We have already discussed balanced and unbalanced delta-connected, three-phase, resistance loads, but let's now turn our attention to wye-connected loads.

Wye-Connected, Three-Phase, Resistance Loads

Let's start by looking at balanced, wye-connected, three-phase, resistive loads, then we will move on to unbalanced, wye-connected, three-phase, resistive loads in a later section.

Balanced, Wye-Connected, Three-Phase, Resistance Loads without Neutral Connection

Figure 10 below shows a balanced, three-phase load connected in wye and powered by a 480 V, 3-phase, 3-wire delta source, without a neutral connection. We simply rearranged the three resistance heaters from Figure 4 on page 7 into a wye configuration. They were each 10 KW in Figure 4, but that is not true when they are arranged as shown in Figure 10. As discussed earlier, this is known as a balanced, three-phase load because all three of the loads are equal to each other: 23 Ω , in this example. Since the loads are connected in wye with 480V applied to the outside connections, there is only 277 V across each resistance. This was illustrated in Figure 1 on page 4.

When 277 V is applied across 23 Ω , the current will be $277 \text{ V} / 23 \Omega = 12 \text{ A}$. The power across each resistance will be $277 \text{ V} * 12 \text{ A} = 3,324 \text{ W}$. Since there are three 3,324 W loads, the total load is 9,972 W, which is nominally 10 KW worth of load in Figure 10 below. When calculating the current flow to a balanced 10 KW load at an applied voltage of 480 V, three-phase, we simply divide the total load by the applied line-to-line voltage and the square root of three, thusly: $10,000 \text{ W} / (480\text{V} * \sqrt{3}) = 12 \text{ A}$. Notice that the line current, such as I_a , is equal to the phase current inside the wye, namely I_{an} . Notice, also, that the line current for the same load

(23 Ω per phase) connected in wye is one-third (1/3) of that same load when connected in delta. This is because:

1. The voltage across each of the three resistances is only $480 \text{ V} / \sqrt{3} = 277 \text{ V}$ when connected in wye;
2. The resulting current through each of the three resistances at this voltage is the $(480 \text{ V current}) / \sqrt{3} = 20.8 \text{ A} / \sqrt{3} = 12 \text{ A}$; and
3. The phase current is the same as the line current, which is 12 A in this example, rather than 36 A (nominally) in Figure 7 on page 9.

As can be seen, the square root of three comes into play twice in the first two line items above to make a combined ratio of $1/\sqrt{3} * 1/\sqrt{3} = 1/3$. Another aspect of this wye-delta relationship is that the input resistance of a wye-connected balanced load is three times the input resistance of a delta-connected balanced load, as illustrated in Figure 24 in PDH Online Course *E413 Wye-Delta Motor Starters*, listed in the Additional Reading section beginning on page 24.

The information just discussed reinforces the ratio of power to the square of the applied voltage – namely, the ratio = $(277)^2 : (480)^2 = 76,729 : 230,400 = 0.333 : 1 = 1 : 3 = 10 \text{ KW} : 30 \text{ KW}$.

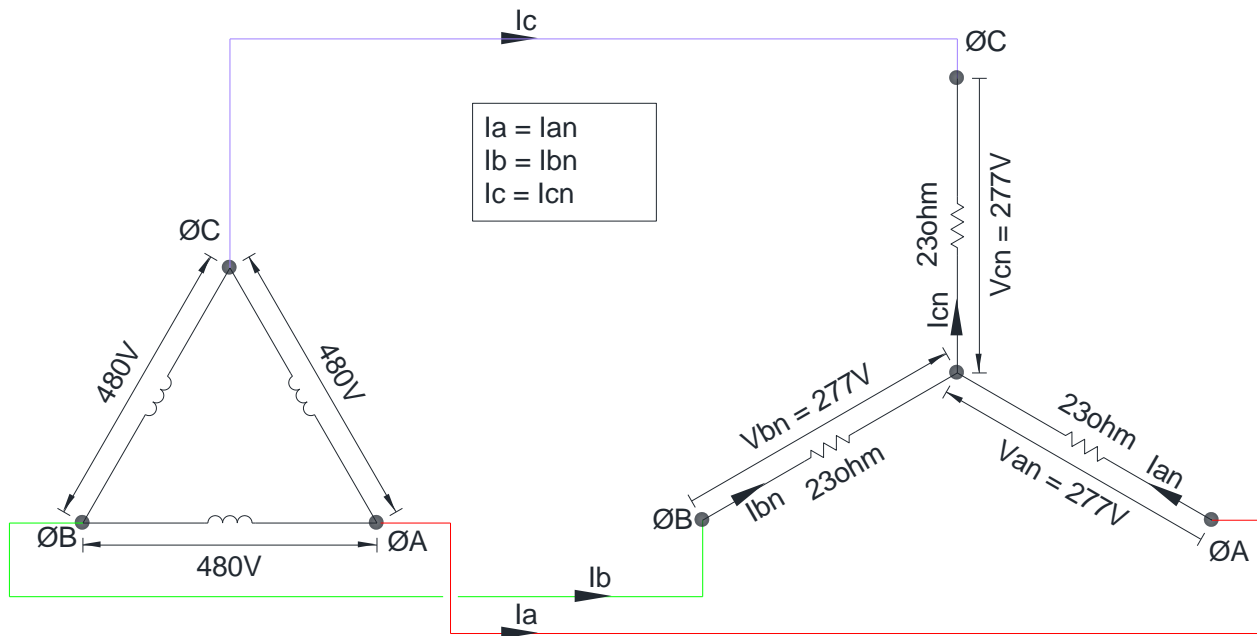


Figure 10 – 10 KW, Balanced, Wye-Connected, Three-Phase, Resistance Load, without Neutral Connection

Figure 10 does not show a neutral connection, and, for a balanced, wye-connected, three-phase load, there would not be any neutral current. See Figure 12 below for the phase and neutral currents. Let’s add a neutral conductor, nonetheless, in the next section.

Balanced, Wye-Connected, Three-Phase, Resistance Loads with Neutral Connection

As seen in Figure 11 below, the neutral current (I_n) is equal to the vector sum of the phase-currents, which is the same as the sum of the line currents ($I_a + I_b + I_c$). Since, in a balanced, three-phase circuit, all three of the line currents are of equal amplitude and 120° apart, they add up to zero, as illustrated in Figure 12.

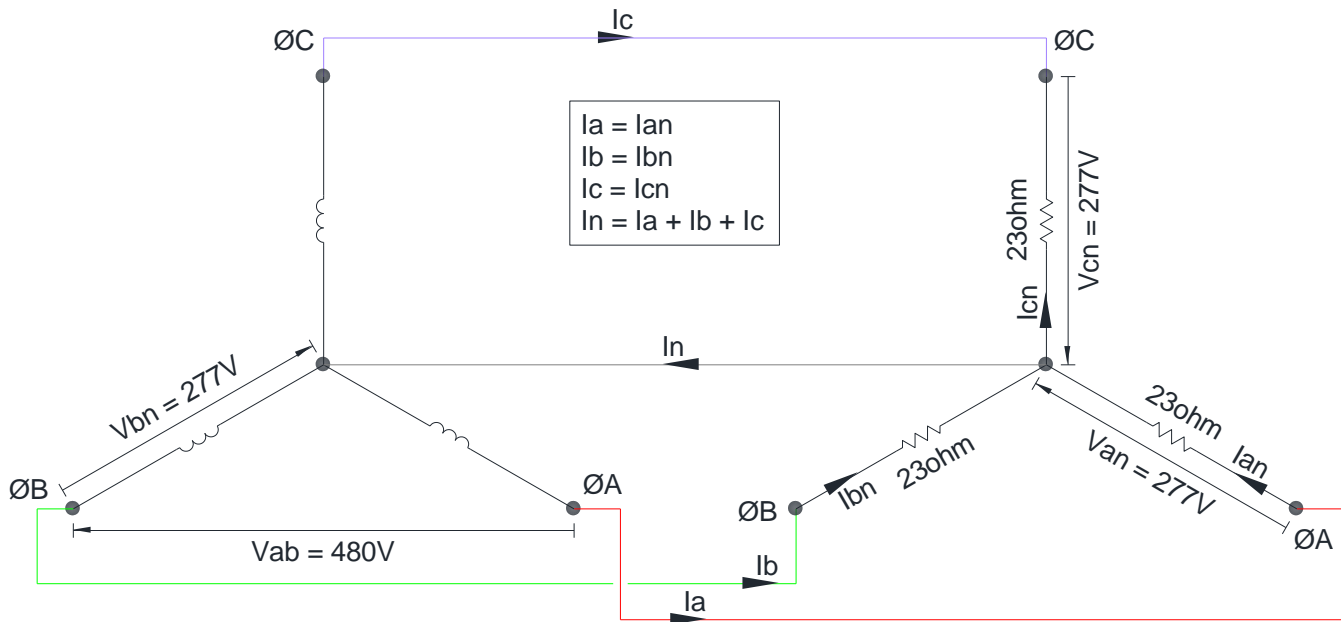


Figure 11 – 10 KW, Balanced, Wye-Connected, Three-Phase, Resistance Load, with Neutral Connection

It can be seen from the right-hand side of Figure 12 below that the neutral current (I_n) is equal to zero because it is the vector sum of the line currents ($I_a + I_b + I_c$), which add up vectorially to zero. In other words, starting at the beginning of vector I_{an} and working to the arrowhead of that vector, then adding vector I_{bn} , then adding vector I_{cn} , brings us back to our starting point at the beginning of vector I_{an} , resulting in a total neutral current of zero.

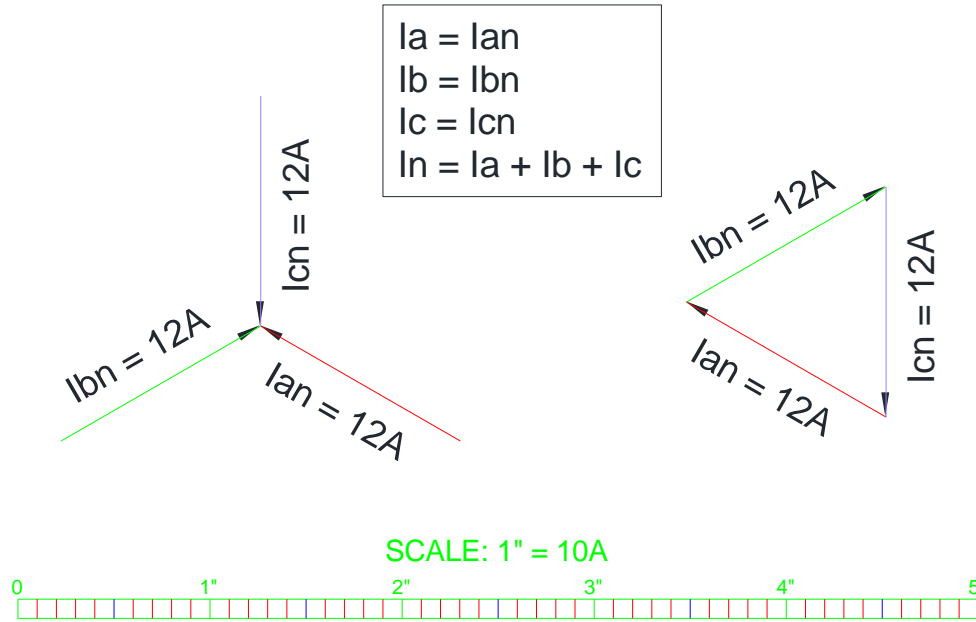


Figure 12 - 10 KW, Balanced, Wye-Connected, Three-Phase Load at 480 V

Let's consider the unbalanced loads shown previously in Figure 8 on page 10, but connected in wye instead of in delta.

Unbalanced, Wye-Connected, Three-Phase, Resistance Loads with Neutral Connection

We will include a neutral connection to carry the unbalanced current, as shown in Figure 13 below. Since the neutral conductor is present, it will keep the center of the wye-connected load at the same potential as the center of the wye-connected power source, assuming zero resistance in the neutral conductor. This means the center of the wye-connected load will have a potential difference of 277 V with regard to the three different phase connections, regardless of the unbalanced load resistance values. The center of the wye-connected power source is almost always grounded in most installations, but we are ignoring that in Figure 13.

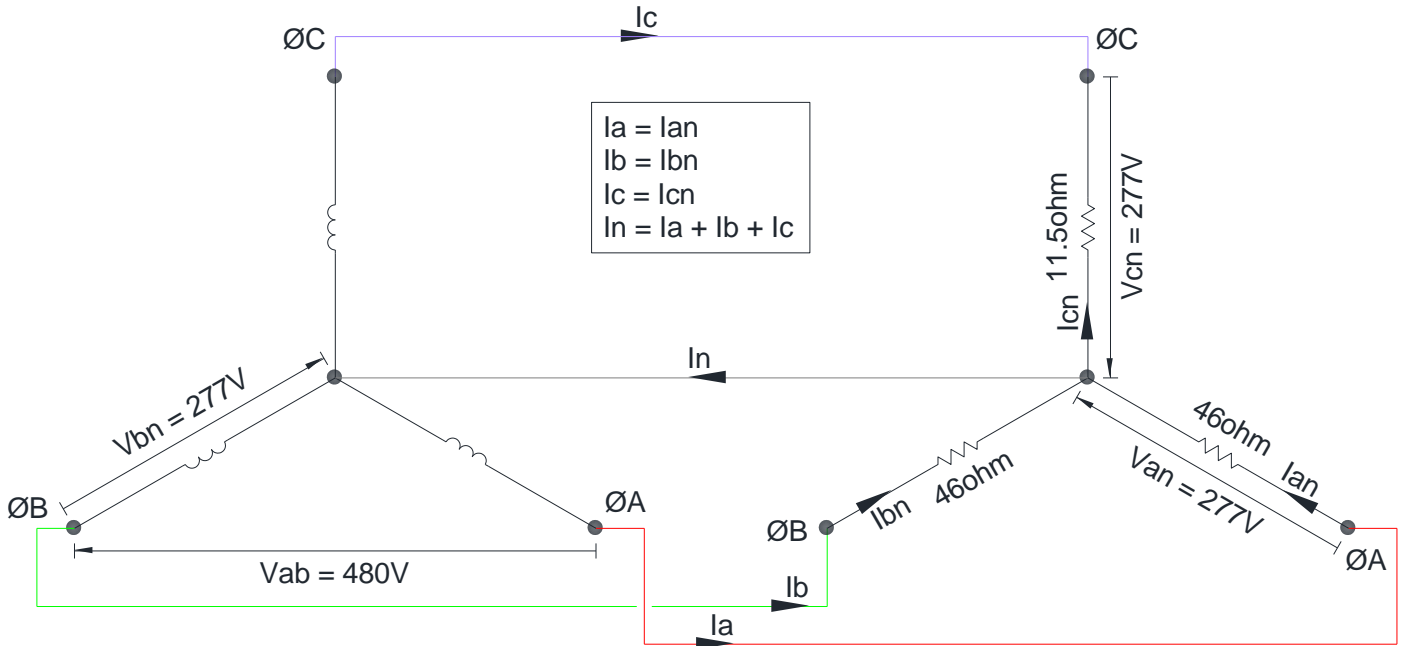


Figure 13 – 10 KW, Unbalanced, Wye-Connected, Three-Phase, Resistance Load, with Neutral Connection

The 11.5 Ω resistance from phase C to neutral will have 277 V applied to it, resulting in a phase current and line current equal to $277 \text{ V} / 11.5 \text{ } \Omega = 24.1 \text{ A}$. Both of the 46 Ω resistances, with 277 V across them, will have a current of $277 \text{ V} / 46 \text{ } \Omega = 6 \text{ A}$ flowing through them, in a vector direction determined by the applied voltage, as shown in Figure 14 below.

The neutral current (I_n) is equal to the vector sum of the phase-currents, which is the same as the sum of the line currents ($I_a + I_b + I_c$). Since this is an unbalanced, three-phase load, the unbalanced current will flow through the neutral conductor back to the source. If the Reader desires an equation for the neutral current, it is:

$$N = \sqrt{(A^2 + B^2 + C^2 - AB - BC - CA)}$$

Where: N = the magnitude of neutral current I_n ;

A = the magnitude of line current I_{an} ;

B = the magnitude of line current I_{bn} ;

C = the magnitude of line current I_{cn} .

Plugging in the line current values that we just calculated into the formula above will yield the same result for the neutral current I_n as illustrated in Figure 14 below. It is clear from the formula that the neutral current would be zero if $A = B = C$.

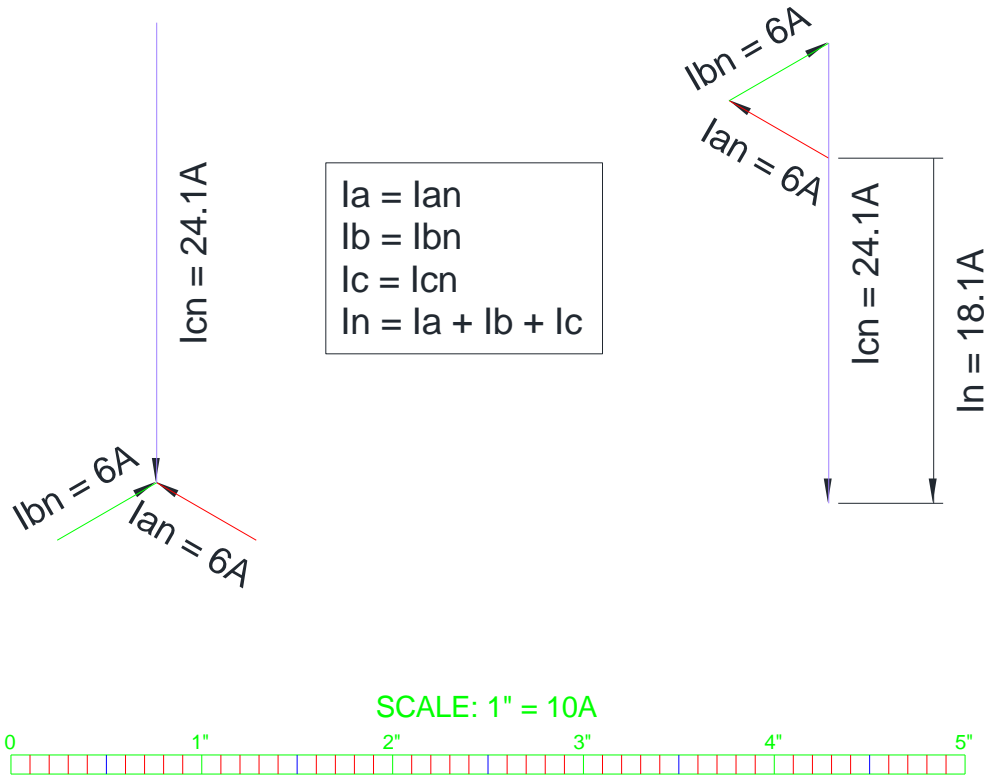


Figure 14 - 10 KW, Unbalanced, Wye-Connected, Three-Phase, Resistance Load at 480 V


We have looked at the square root of three from the perspective of the load, but now let's take a look at the power source.

√3 In Three-Phase Transformer Banks


The square root of three determines the amount of KVA and current that can be provided by a three-phase enclosed transformer or three-phase transformer bank. The two arrangements of transformer windings that will be discussed in this section are closed-delta and open-delta.

Closed-Delta Transformer Banks

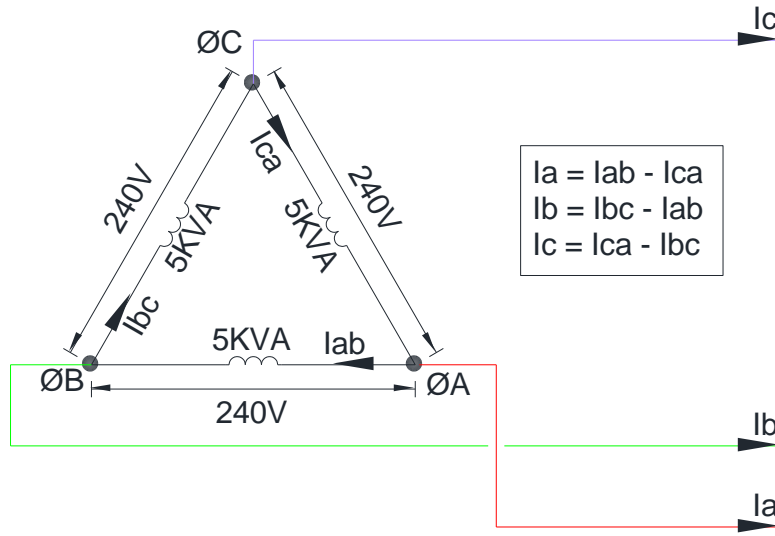A closed-delta transformer bank is shown in Figure 15(a) below. Each of the three legs is a 5 KVA single-phase transformer, and the transformer bank or enclosed transformer provides 15 KVA when connected as a closed delta, as shown in that figure.





(a) Closed-Delta

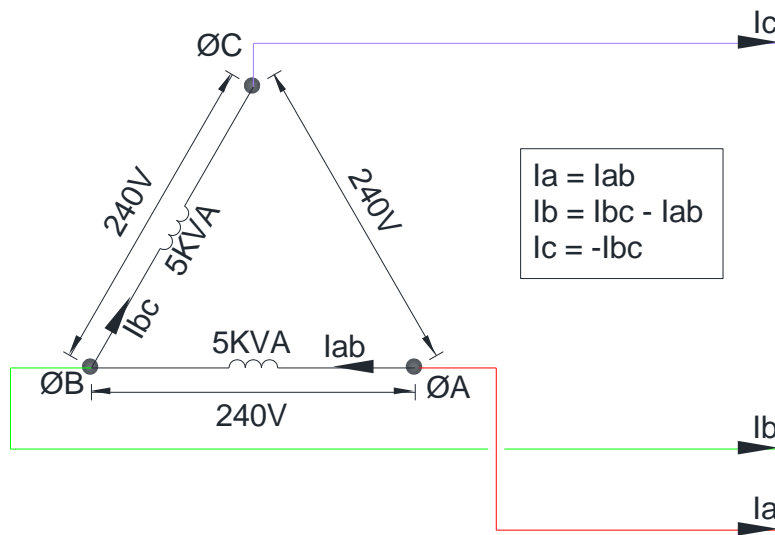

(b) Open-Delta



Figure 15 – Three-Phase Delta-Connected Transformer Banks at 240 V

As was seen earlier for a balanced, delta-connected, three-phase resistance load in Figure 4 on page 7 and Figure 7 on page 9, the line currents are equal to $\sqrt{3}$ times the phase currents inside of the delta. The same is true for a closed-delta three-phase transformer bank when the KVA ratings of all three transformers are the same. The amount of current that each of the 5 KVA single-phase transformers can provide is $5,000 \text{ VA} / 240 \text{ V} = 20.83 \text{ A}$. That is the maximum current through each transformer inside of the delta. When these delta currents are combined into line currents on the way to the load, the maximum line current that the closed-delta transformer bank can provide is $\sqrt{3}$ times the winding current or $20.83 \text{ A} * \sqrt{3} = 36.08 \text{ A}$. This is shown for the line current I_a in Figure 16(a) below, which is reminiscent of Figure 7 on page 9.

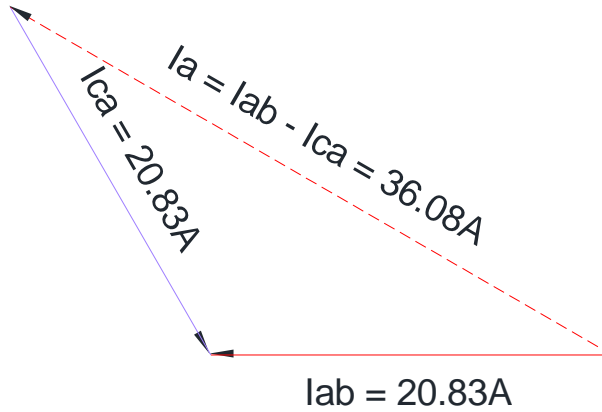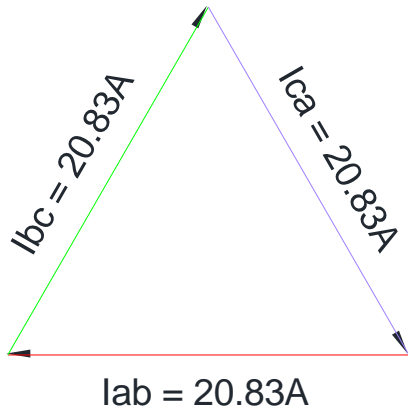

$I_a = I_{ab} - I_{ca}$
 $I_b = I_{bc} - I_{ab}$
 $I_c = I_{ca} - I_{bc}$

(a) Closed-Delta

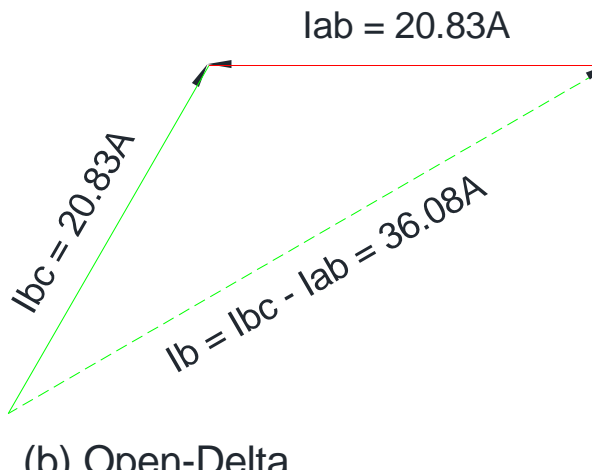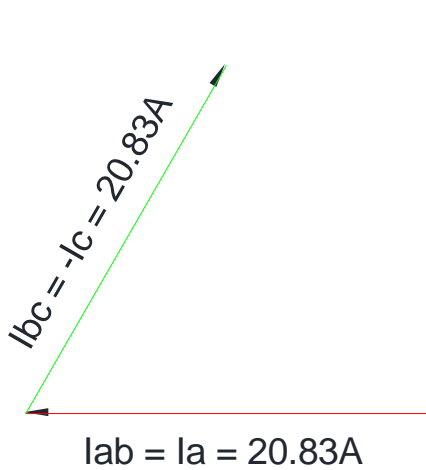

$I_a = I_{ab}$
 $I_b = I_{bc} - I_{ab}$
 $I_c = -I_{bc}$

(b) Open-Delta

SCALE: 1" = 10A



Figure 16 - Currents in Three-Phase Delta-Connected Transformer Banks at 240 V

Now that we have determined the amount of KVA and line current available from a closed-delta three-phase transformer, let's see what happens when one of the transformers is removed, thus creating an open-delta transformer bank.

Open-Delta Transformer Banks

Figure 15(b) on page 19 shows the open-delta three-phase transformer bank that results when one of the transformers from the closed-delta three-phase transformer bank is removed. As can be seen in that figure, the maximum line currents I_a and I_c are equal to the winding currents inside the transformer, or 20.83 A, as shown in Figure 16(b). From that figure, the maximum line current I_b might seem like it has more available than I_a and I_c , but I_b is the current returning from the loads connected to Phase A and Phase C. In other words, the most current you can provide to any load, whether connected A-B, B-C, or C-A, is 20.83 A. This can be visualized mentally or drawn by hand on Figure 15(b) on page 19. If a load is connected between Phase A and Phase B, the maximum current that can be provided by the winding between those phases is 20.83 A. Likewise, if a load is connected between Phase B and Phase C, the maximum current that can be provided by the winding between those phases is 20.83 A. Finally, if a load is connected between Phase C and Phase A, the current passes through both of the windings, and that current is still limited to 20.83 A. As we have seen above, this current is related to the line current of a closed-delta three-phase transformer bank by $1 / \sqrt{3}$. The Reader might see technical documents that say the KVA rating of an open-delta transformer is equal to 58% of the rating of a closed-delta transformer bank, a ratio that is equal to $1 / \sqrt{3}$, the same ratio that was stated for the line currents in the previous sentence. In other words, the 15 KVA rating of the closed-delta three-phase transformer bank in Figure 15(a) would have an open-delta rating of $15 \text{ KVA} / \sqrt{3} = 8.66 \text{ KVA}$ in Figure 15(b).

The Reader might sometimes see the ratio of KVA ratings for open-delta transformer banks to be 87% of the rating of the two transformers, but this works out to be the same as 58% of the rating of the three transformers. That is, $10 \text{ KVA} * 87\% = 8.66 \text{ KVA}$. The ubiquitous square root of three still appears in this 87% ratio for open-delta transformer KVA ratings, since 87% is the result of $\sqrt{3} / 2$.

To phrase it yet another way, the KVA rating of the open-delta transformer bank is equal to $\sqrt{3}$ times the KVA rating of one transformer, or $\sqrt{3} * 5 \text{ KVA} = 8.66 \text{ KVA}$.

Thus far, we have considered transformer banks in which all of the individual transformers are identical. Sometimes, one of the transformers in an open-delta transformer bank is center-tapped to provide 240/120V single-phase power to receptacles and other single-phase loads.

This transformer is often larger than the other transformer in order to accommodate its single-phase and three-phase dual functions. Consider Figure 15(b) on page 19 and imagine that the larger of the two transformers is installed between Phase A and Phase B. This would provide additional current for loads connected between Phase A and Phase B, but would not provide additional current to loads connected between Phase B and Phase C or between Phase C and Phase A.

What is a transformer bank?

A transformer bank is comprised of two or more single-phase transformers wired together, typically to provide three-phase power.

Interested Readers can see *PDH Online Course E427 Standard AC System Voltages (600V and Less)*, listed in the Additional Reading section beginning on page 24 for further discussion of transformer arrangements, connections, and voltages.

$\sqrt{3}$ In Three-Phase Voltage-Drop Calculations

The square-root of three ($\sqrt{3}$) is used in voltage-drop calculations for balanced three-phase circuits, such as in this common voltage drop formula:

$$V_{\text{drop}} = \sqrt{3} * R * I * L$$

where: R = conductor ohms-to-neutral per 1,000 ft

I = line current

L = one-way conductor length for one conductor

Why is the square root of three included in this calculation? It is because the line-to-line (phase-to-phase) resistance is related to the line-to-neutral (phase-to-neutral) resistance by the square root of three, the same relationship that was illustrated in Figure 1 on page 4. This is most easily demonstrated by confirming the measurements shown in Figure 17 below. The line-to-neutral supply voltage is 3 V, so the line-to-line supply voltage is $\sqrt{3}$ times that, or 5.196 V, as can be directly measured in that figure with reasonable accuracy.

Actual Voltage Drops Are:

Line-to-Neutral: $3V - 2.5V = 0.5V$

Line-to-Line: $5.196V - 4.330V = 0.866V = 0.5V * \text{SQRT}(3)$

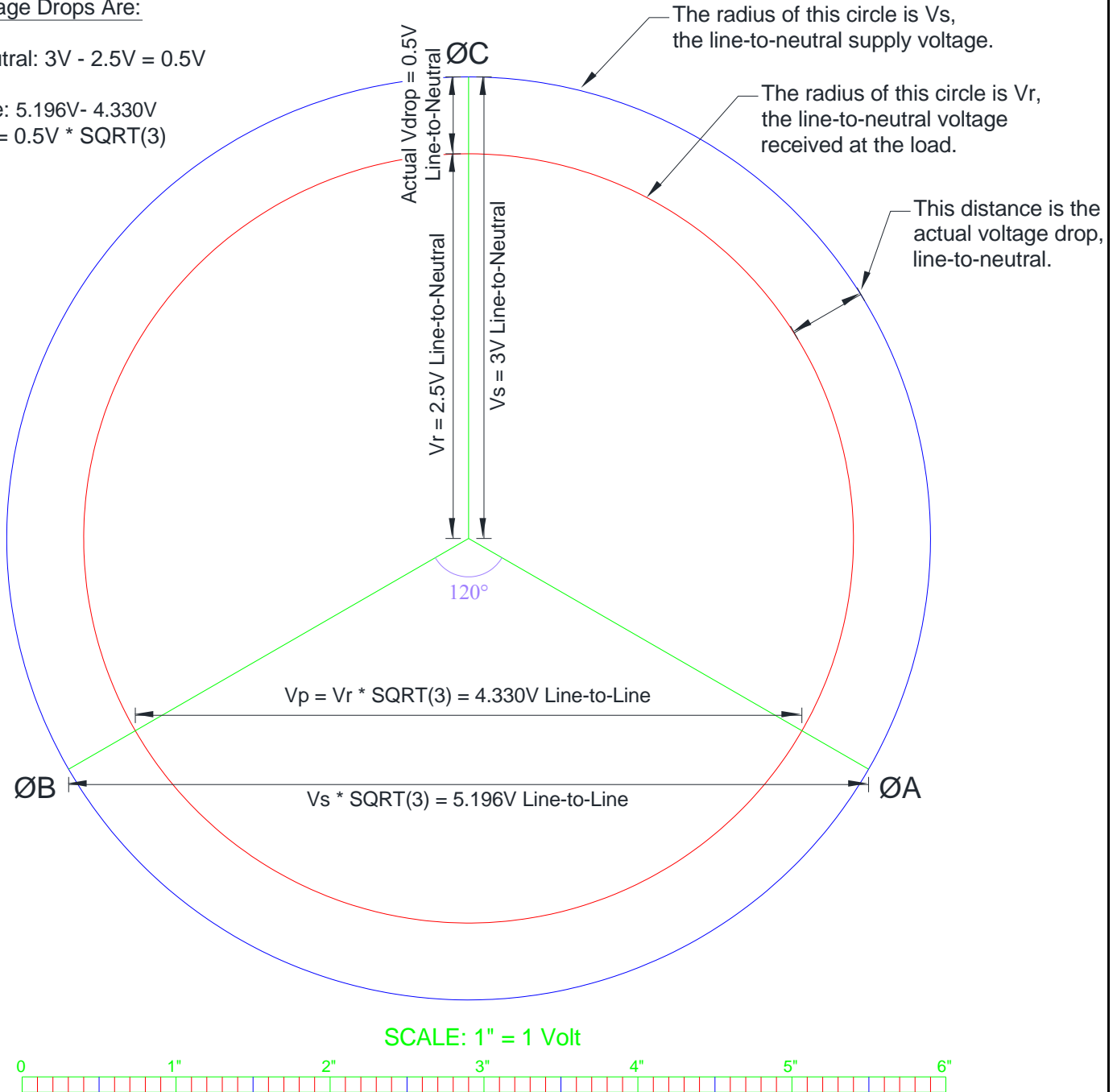


Figure 17 - The Square Root of Three in Balanced Three-Phase Voltage-Drop Calculations

As can be seen in Figure 17, there is nothing mystical or magical about using the square root of three in balanced three-phase voltage drop calculations – it is based on simple geometry. If the line-to-neutral voltage drop is 0.5 V, then the line-to-line voltage drop is $\sqrt{3}$ times that or 0.866 V. Confirm this by measuring the line-to-line voltages V_s (5.196 V) and V_r (4.330 V) to see that the line-to-line difference, the line-to-line voltage drop, is 0.866 V. Draw it in a CAD program for maximum accuracy to confirm the measurements.

The three-phase voltage drop formula at the beginning of this section is used by many people, and it is a reasonable approximation of voltage drop, but there is a more accurate formula to obtain the Actual voltage drop. Interested Readers can peruse PDH Online course *E426 Voltage Drop Calculations*, listed in the section Additional Reading beginning on page 24.

In Closing

The square root of three is used every day in several types of three-phase electrical calculations, though not everyone understands the reasons why. The square root of three is applicable to a variety of balanced three-phase circuits and calculations, but usually not to unbalanced three-phase circuits and calculations.

Abbreviations

- A Amp or Amps
- AC Alternating Current
- N.A. Not Applicable
- V Volt or Volts
- VAC Volts Alternating Current

Additional Reading

PDH Online course E336 Calculating Currents in Balanced and Unbalanced Three Phase Circuits at www.pdhonline.org

PDH Online course E413 Wye-Delta Motor Starters at www.pdhonline.org

PDH Online course E426 Voltage Drop Calculations at www.pdhonline.org

PDH Online course E427 Standard AC System Voltages (600 V and Less) at www.pdhonline.org

